


Name: Micah Perkins

EECE.2650 Logic Design


Assignment 4

State Diagram:

even_odd = 1

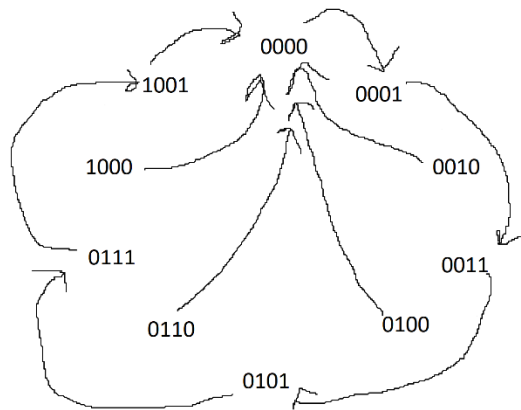

even_odd = 0

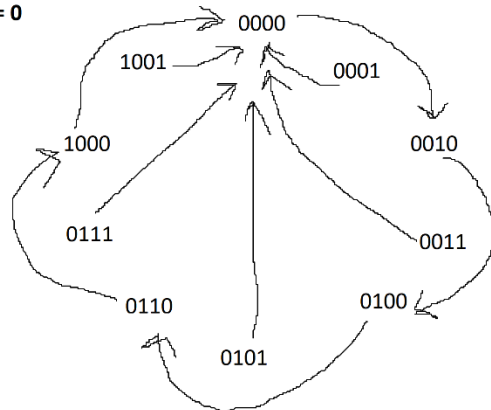

10-15 are don't-care conditions

State/Transition Table:

PS ($Q_3Q_2Q_1Q_0$)	NS ($Q_3^+Q_2^+Q_1^+Q_0^+$)	
	even_odd = 0	even_odd = 1
0 0 0 0	0 0 1 0	0 0 0 1
0 0 0 1	0 0 0 0	0 0 1 1
0 0 1 0	0 1 0 0	0 0 0 1
0 0 1 1	0 0 0 0	0 1 0 1
0 1 0 0	0 1 1 0	0 0 0 1
0 1 0 1	0 0 0 0	0 1 1 1
0 1 1 0	1 0 0 0	0 0 0 1
0 1 1 1	0 0 0 0	1 0 0 1
1 0 0 0	0 0 0 0	0 0 0 1
1 0 0 1	0 0 0 0	0 0 0 1
1 0 1 0	0000 (Don't care)	0001 (Don't care)
1 0 1 1	0000 (Don't care)	0001 (Don't care)
1 1 0 0	0000 (Don't care)	0001 (Don't care)
1 1 0 1	0000 (Don't care)	0001 (Don't care)
1 1 1 0	0000 (Don't care)	0001 (Don't care)
1 1 1 1	0000 (Don't care)	0001 (Don't care)

$$Q_3^+_{\text{even_odd} = 0} = \text{SUMOF } m(6) + d(14)$$

$$Q_3^+_{\text{even_odd} = 1} = \text{SUMOF } m(7) + d(15)$$

$$Q_2^+_{\text{even_odd} = 0} = \text{SUMOF } m(2, 4) + d(10, 12)$$

$$Q_2^+_{\text{even_odd} = 1} = \text{SUMOF } m(3, 5) + d(11, 13)$$

$$Q_1^+_{\text{even_odd} = 0} = \text{SUMOF } m(0, 4)$$

$$Q_1^+_{\text{even_odd} = 1} = \text{SUMOF } m(1, 5)$$

$$Q_0^+_{\text{even_odd} = 0} = 0$$

$$Q_0^+_{\text{even_odd} = 1} = \text{SUMOF } m(0, 1, 2, 3, 4, 5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15) = 1$$

KMAPS:

Q_3^+

Q_1Q_0		00	01	11	10
Q_3Q_2	00	0	0	0	0
	01	0	0	0	1
	11	d	d	d	d
	10	0	0	d	d

even_odd = 0

Q_1Q_0		00	01	11	10
Q_3Q_2	00	0	0	0	0
	01	0	0	1	0
	11	d	d	d	d
	10	0	0	d	d

even_odd = 1

Q_2^+

Q_1Q_0		00	01	11	10
Q_3Q_2	00	0	0	0	1
	01	1	0	0	0
	11	d	d	d	d
	10	0	0	d	d

even_odd = 0

Q_1Q_0		00	01	11	10
Q_3Q_2	00	0	0	1	0
	01	0	1	0	0
	11	d	d	d	d
	10	0	0	d	d

even_odd = 1

Q_1^+

Q_1Q_0		00	01	11	10
Q_3Q_2	00	1	0	0	0
	01	1	0	0	0
	11	d	d	d	d
	10	0	0	d	d

even_odd = 0

Q_1Q_0		00	01	11	10
Q_3Q_2	00	0	1	0	0
	01	0	1	0	0
	11	d	d	d	d
	10	0	0	d	d

even_odd = 1

Q_0^+

Q_1Q_0		00	01	11	10
Q_3Q_2	00	0	0	0	0
	01	0	0	0	0
	11	d	d	d	d
	10	0	0	d	d

even_odd = 0

Q_1Q_0		00	01	11	10
Q_3Q_2	00	1	1	1	1
	01	1	1	1	1
	11	d	d	d	d
	10	1	1	d	d

even_odd = 1

Minimal SOP for DFFs:

$$Q_3^+ = (Q_2 \text{ AND } Q_1) \text{ AND } (\text{even_odd XNOR } Q_0)$$

$$Q_2^+ = (Q_2 \text{ XOR } Q_1) \text{ AND } (\text{even_odd XNOR } Q_0)$$

$$Q_1^+ = (\text{NOT}(Q_3) \text{ AND } \text{NOT}(Q_1)) \text{ AND } (\text{even_odd XNOR } Q_0)$$

$$Q_0^+ = \text{even_odd}$$

Block Diagram and Simulation Result: (make sure your filename path is readable in your screenshots)

