

## Objective:

The objective of this assignment is to design an ALU (Arithmetic Logic Unit).

## PART I. Design

### Design Specifications:

Design an Arithmetic Logic Unit that performs a set of operations on up to two 4-bit binary numbers based on a 3-bit operation code (OpCode).

### Inputs:

clk: clock input, 10ns period 50% duty-cycle

DataA[3..0]: 4-bits of Data

DataB[3..0]: 4-bits of Data

RESET: Active low reset that sets the ALU to an initial state, with all data set to zero.

OpCode[2..0]: 3-bit Control input that represents a code for each operation.

START: 1-bit Control input that starts the operation after the OpCode has been set.

### Outputs:


Q[3..0]: 4-bit result (Q3 is the MSB)

### ALU Function Set

OpCode	Function
000	$A + B$ (addition)
001	$A + 1$ (increment by 1)
010	$\sim A$ (Compliment A)
011	$B - A$ (subtraction)
100	$A - 1$ (decrement by 1)
101	$A \mid B$ (bitwise OR)
110	$A \& B$ (bitwise AND)
111	$-A$ (Mathematical Negative A)

**Design:** The design will consist of 3 modules: A Data Path, a State Generator, and a Control Circuit. The final circuit will connect these three modules to the inputs and outputs listed above. **Each of the following sections should be its own bdf file.**

## Data Path:

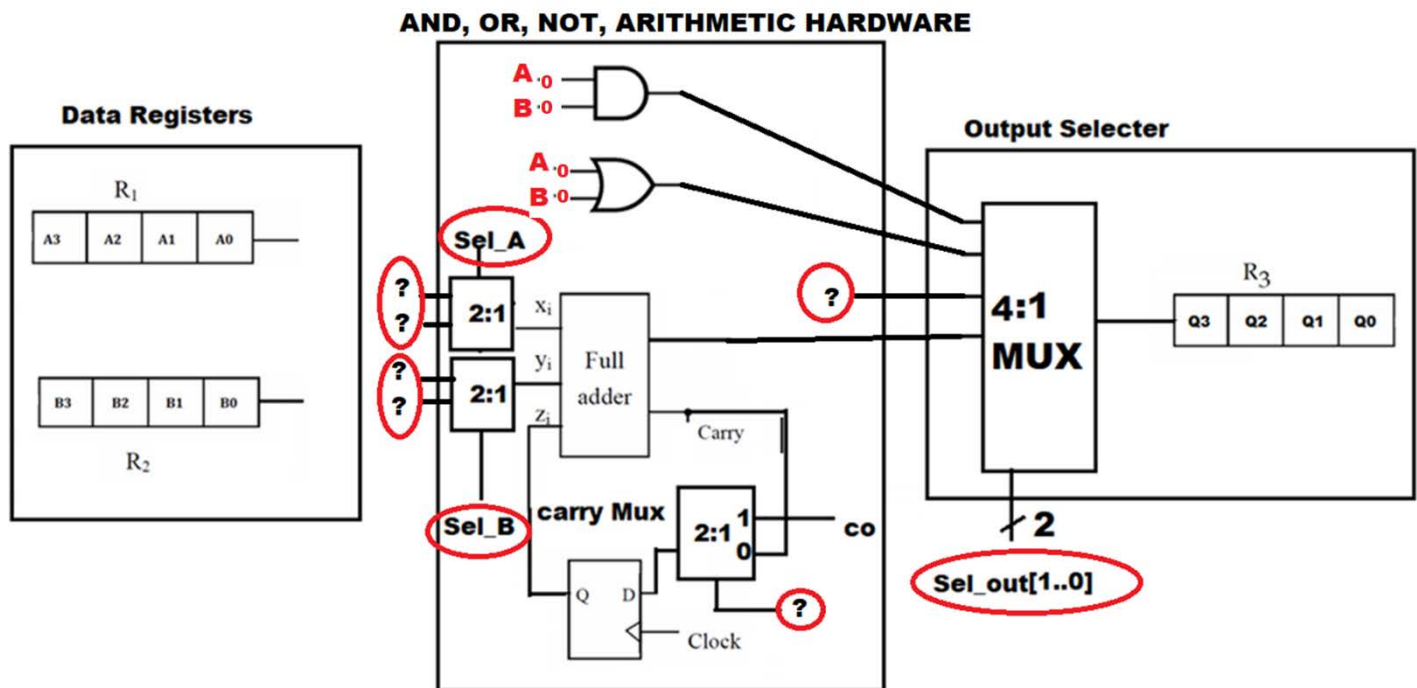

## Data Path Hardware:

THREE universal shift/parallel load registers (74194) : R1,R2,R3

ONE 1-bit Full adder (from Assignment 2)

ONE D-Type FF (for the carry)

Unlimited AND, OR, NOT, XOR, XNOR Gates

ONE 4:1 Multiplexer (74153M in Quartus – see details in the *Specialized Chips* section)

THREE 2:1 Multiplexers (21mux in Quartus)

## Data Path Inputs:

S1, S0, RESET, clk,

DataA[3..0], DataB[3..0]

Sel\_A, Sel\_B, Sel\_out[1..0] (select bits for each MUX)

c0 (Initial carry for the serial adder)

const – a variable that can be set to a 1 or 0

## Data Path Outputs:

Q[3..0]

**State Generator:** The State Generator should be designed to cycle through each state of the operation. Since these are 4-bit numbers, the operation will need at least 5 clock cycles, Load + 4 shift operations.

**State Generator Behavior:**

Hold in the initial state (T0) until START is set to 1

Perform the operation by shifting the data through the data path.

Wait until START is set back to 0 before returning to the initial state.

Asynchronously return to the initial state (T0) when the system RESET is pushed

**State Generator Hardware:**

For the state generator you should use 6 States with 1-hot encoding.

You can utilize the following chips:

Unlimited AND, OR, NOT, XOR, XNOR Gates

6 DFF

**State Gen Inputs:**

RESET

START

clk

**State Gen Outputs:**

T[0..5] – present state

**Control Circuit:** The Control Circuit is a purely combinational circuit that will take the user inputs and translate them into signals for the Data Path and the State Generator.

**Control Circuit Inputs:**

T[0..5]

START

OpCode[2..0]

**Control Circuit Outputs:**

S1, S0


Sel\_A, Sel\_B, Sel\_out[1..0]

c0, const

**Control Circuit Hardware:**

Unlimited AND, OR, NOT, XOR, XNOR Gates


**ASM CHART:**

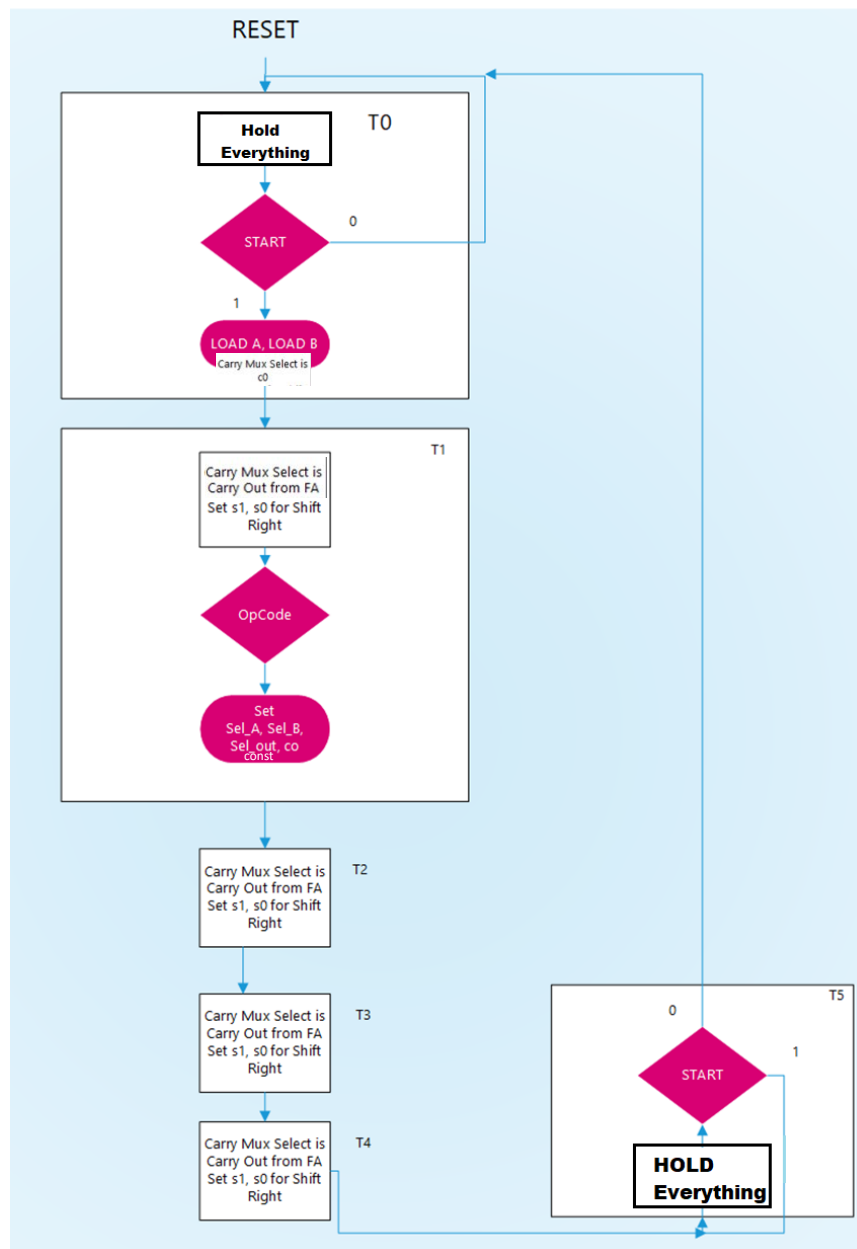

## Specialized Chips used in this design:


### 74153M 4:1 Mux with **ACTIVE\_LOW ENABLE (GN)**

B A	Y
0 0	C0
0 1	C1
1 0	C2
1 1	C3

 

### 74194 Shift Register:

MODE	CLR N	S1	S0	QA	QB	QC	QD
RESET	0	X	X	0	0	0	0
HOLD	1	0	0	QA	QB	QC	QD
SHIFT LEFT	1	1	0	QB	QC	QD	SLSI
SHIFT RIGHT	1	0	1	SRSI	QA	QB	QC
PARALLEL LOAD	1	1	1	A	B	C	D

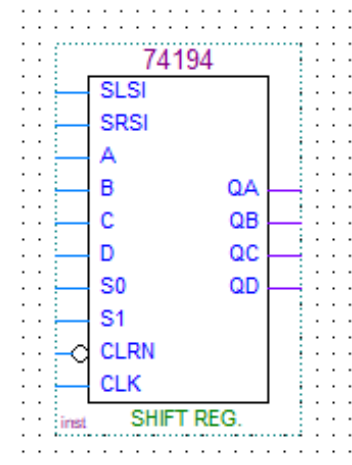

X = Don't care


All transistions except for the asynchronous reset occur on RISING CLOCK EDGE

### DFF is a D-type Flip flop that updates on the Rising Clock Edge:

PRN = asynchronous ACTIVE-LOW PRESET

CLRN = asynchronous ACTIVE-LOW CLEAR

D	Q
0	0
1	1

 


## Final Design:

Take each Block Diagram File for the three circuit modules above and turn them into individual .bsf files

Connect the bsf files in a single bdf as below:

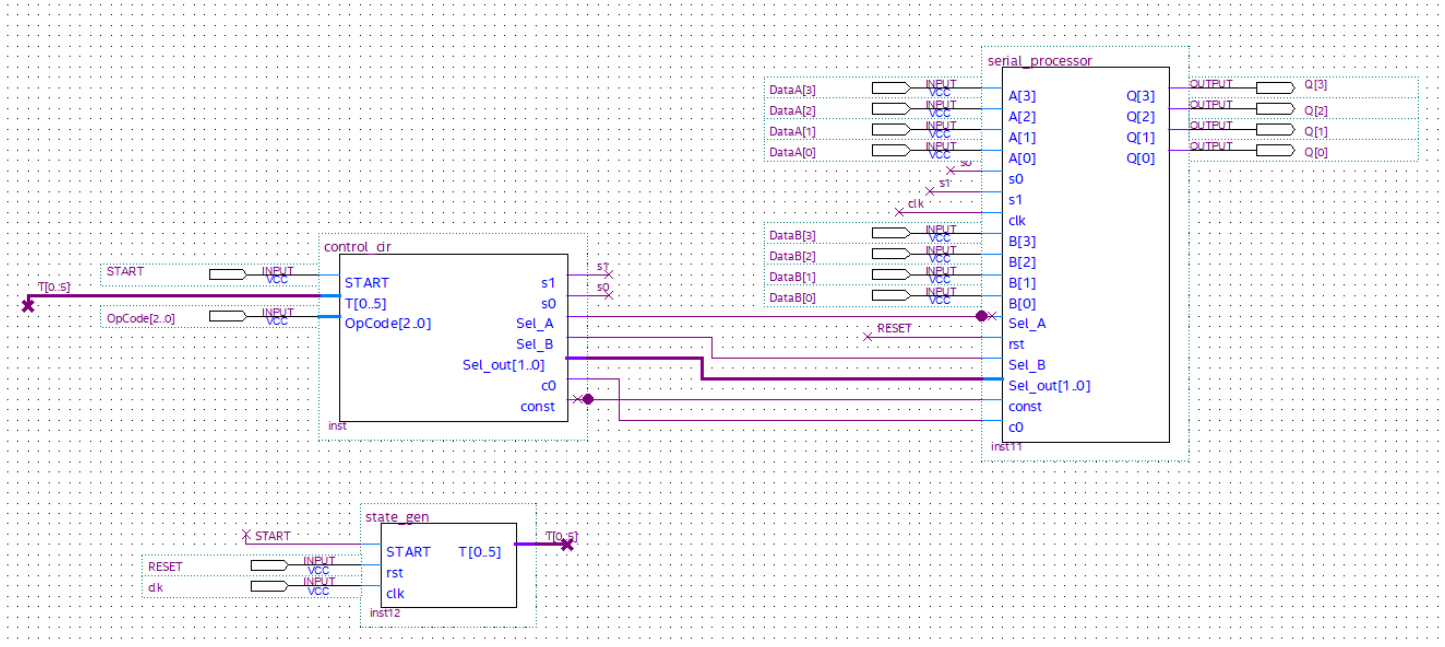**There should be no additional gates in the block diagram.**



**NOTE: The INPUT AND OUTPUT NAMES on this bdf MUST MATCH EXACTLY:**

### Inputs:

clk  
DataA[3..0]  
DataB[3..0]  
RESET  
OpCode[2..0]  
START

### Outputs:

Q[3..0]


Other internal signals, such as Sel\_A, do not need to match exactly.

## Part II: Test

Test each OpCode by doing 8 simulations. Each simulation should last for 100ns.

Set START = 1 from 10ns to 80ns. This way you can make sure that the system is holding in T5 as specified.

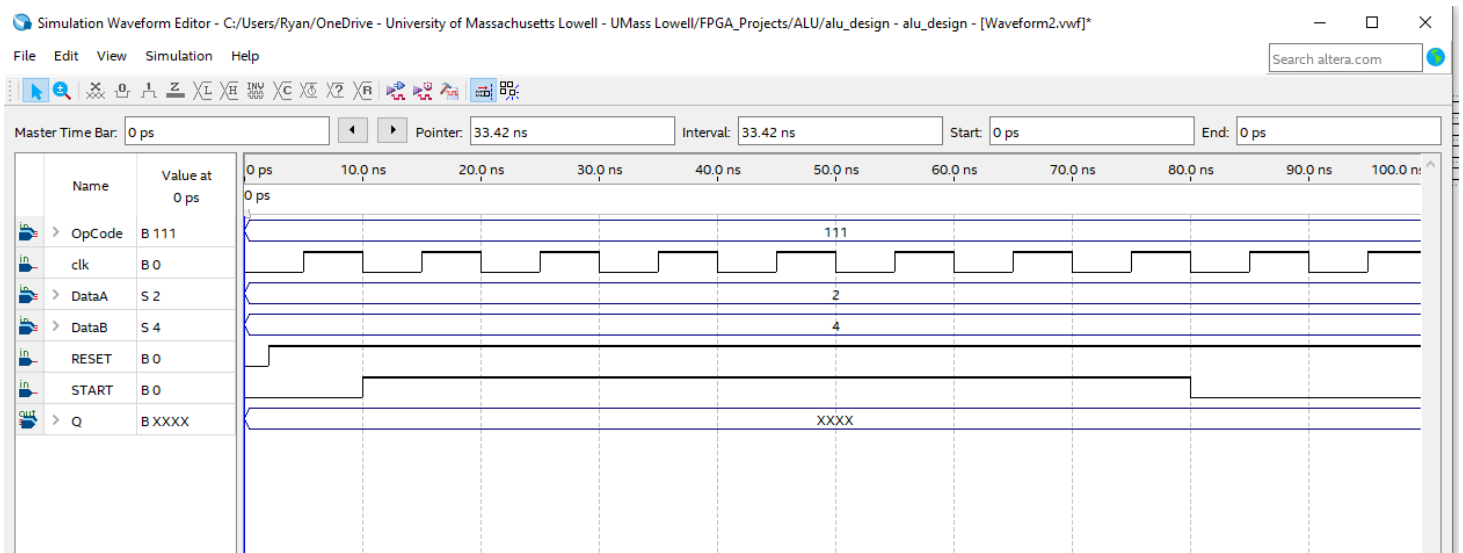Use the template below for your simulations:



You can choose to use whatever numbers you want for A, B. Note that we did not add overflow detection to this circuit.

## Part III: Write-up

Use the separate document, *Assignment 5 Template* for your submission.

## Part IV: What to Submit

You will submit 2 files:

1. The write up (Part III)
2. Your entire project in archived form (.qar file).

**To archive your project, simply go to Project -> Archive Project**  
**The .qar file will be crated in your working directory.**